

My system uses a mux with four options and two select switches. Depending on the switch, it chooses a mode, which each one having its own state transitions that is being incremented or decremented by the clock. However, what takes president during these transitions are the stop/start and reset button. All in all, a simple machine that is invented and used on multiple occasions did not expect to take this much work.

