
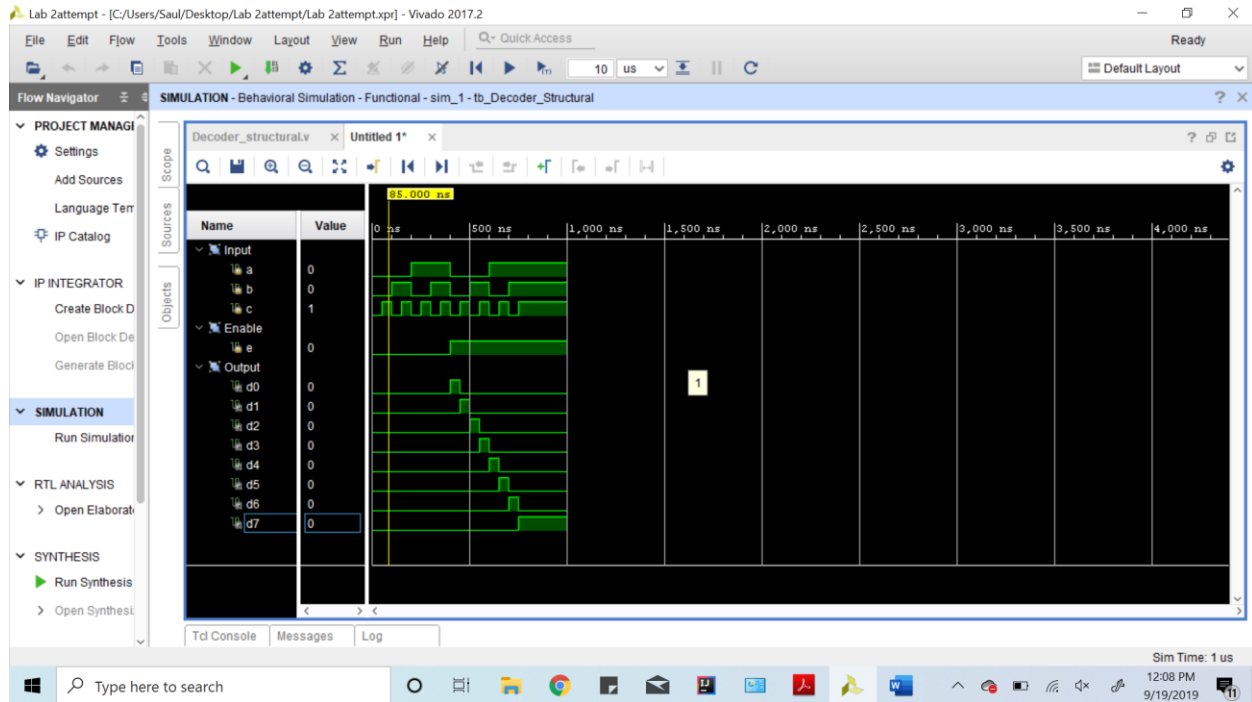


## Part 1

### Decoder\_Structural

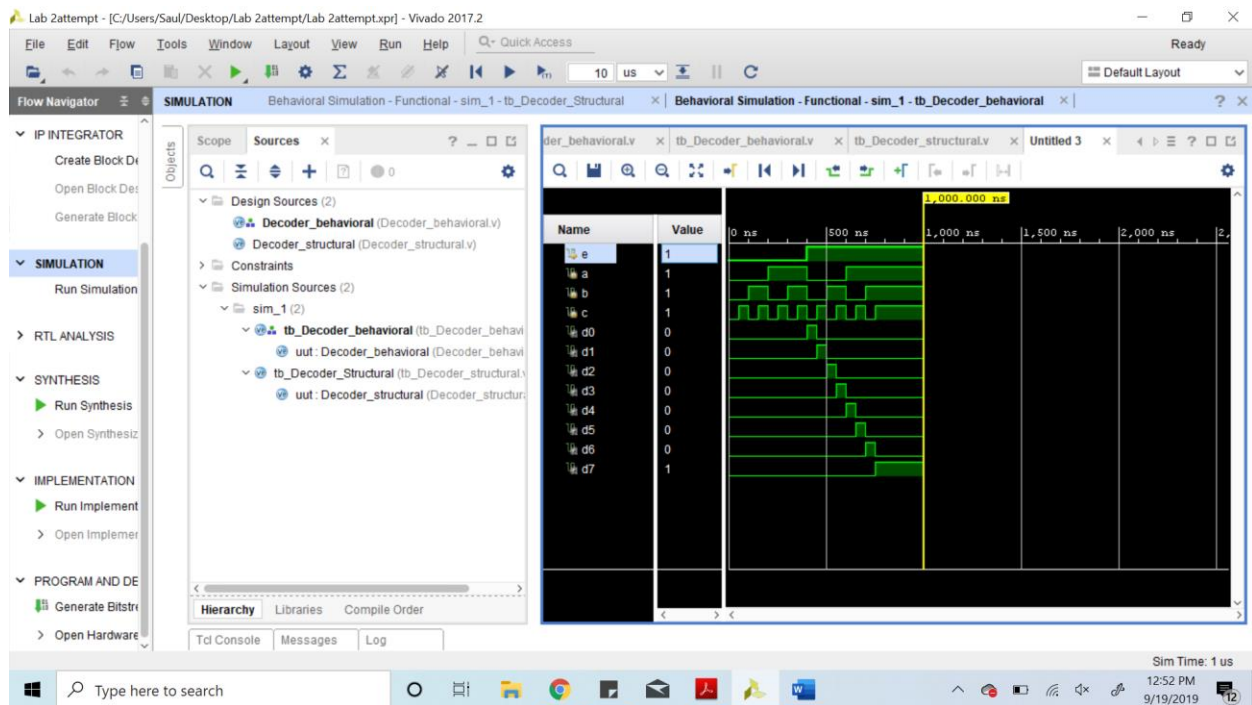

### Decoder\_behavioral



## Part 2

### Design Source: Mux\_structural

```
`timescale 1ns / 1ps
```

```
module Mux_structural(
```

```
    input s0,
```

```
    input s1,
```

```
    input i0,
```

```
    input i1,
```

```
    input i2,
```

```
    input i3,
```

```
    output d
```

```
);
```

```
    wire s0_not, s1_not;
```

```
    not n0 (s0_not, s0);
```

```
    not n1 (s1_not, s1);
```

```
    and g0 (d, s1_not, s0_not);
```

```
    and g1 (d, s1_not, s0);
```

```
    and g2 (d, s1, s0_not);
```

```
    and g3 (d, s1, s0);
```

```
endmodule
```

### **Testbench: tb\_Mux\_Structural**

```
`timescale 1ns / 1ps
```

```
module tb_Mux_Structural;
```

```
    reg i0;
```

```
    reg i1;
```

```
    reg i2;
```

```
    reg i3;
```

```
    reg s1;
```

```
    reg s0;
```

```
    wire d;
```

```
    Mux_behavioral uut (
```

```
        .i0(i0),
```

```
        .i1(i1),
```

```
        .i2(i2),
```

```
        .i3(i3),
```

```
        .s1(s1),
```

```
        .s0(s0),
```

```
        .d(d)
```

```
    );
```

```
    initial begin
```

```
        i0 = 0;
```

```
        i1 = 0;
```

```
i2 = 0;
```

```
i3 = 0;
```

```
s1 = 0;
```

```
s0 = 0;
```

```
#50;
```

```
/* i0 = 0;
```

```
i1 = 0;
```

```
i2 = 0;
```

```
i3 = 0;
```

```
s1 = 0;
```

```
s0 = 0;
```

```
$display ("TC01");
```

```
if (d != 1'b0 ) $display ("Result is wrong");
```

```
#50;
```

```
i0 = 0;
```

```
i1 = 0;
```

```
i2 = 0;
```

```
i3 = 0;
```

```
s1 = 0;
```

```
s0 = 1;
```

```
$display ("TC02");
```

```
if (d != 1'b0 ) $display ("Result is wrong");
```

```
#50;
```

```
i0 = 0;
i1 = 0;
i2 = 0;
i3 = 0;
s1 = 1;
s0 = 0;
$display ("TC03");
if (d != 1'b0 ) $display ("Result is wrong");
#50;
```

```
i0 = 0;
i1 = 0;
i2 = 0;
i3 = 0;
s1 = 1;
s0 = 1;
$display ("TC04");
if (d != 1'b0 ) $display ("Result is wrong");
#50;
```

```
*/
```

```
i0 = 1;
i1 = 0;
i2 = 0;
i3 = 0;
s1 = 0;
s0 = 0;
$display ("TC01");
if (d != 1'b1 ) $display ("Result is wrong");
#50;
```

```
i0 = 0;
i1 = 1;
i2 = 0;
i3 = 0;
s1 = 0;
s0 = 1;
$display ("TC02");
if (d != 1'b1 ) $display ("Result is wrong");
#50;
```

```
i0 = 0;
i1 = 0;
i2 = 1;
i3 = 0;
s1 = 1;
s0 = 0;
$display ("TC03");
if (d != 1'b1 ) $display ("Result is wrong");
#50;
```

```
i0 = 0;
i1 = 0;
i2 = 0;
i3 = 1;
s1 = 1;
s0 = 1;
```

```

$display ("TC04");

if (d != 1'b1 ) $display ("Result is wrong");

```

```


end

```

```

endmodule

```

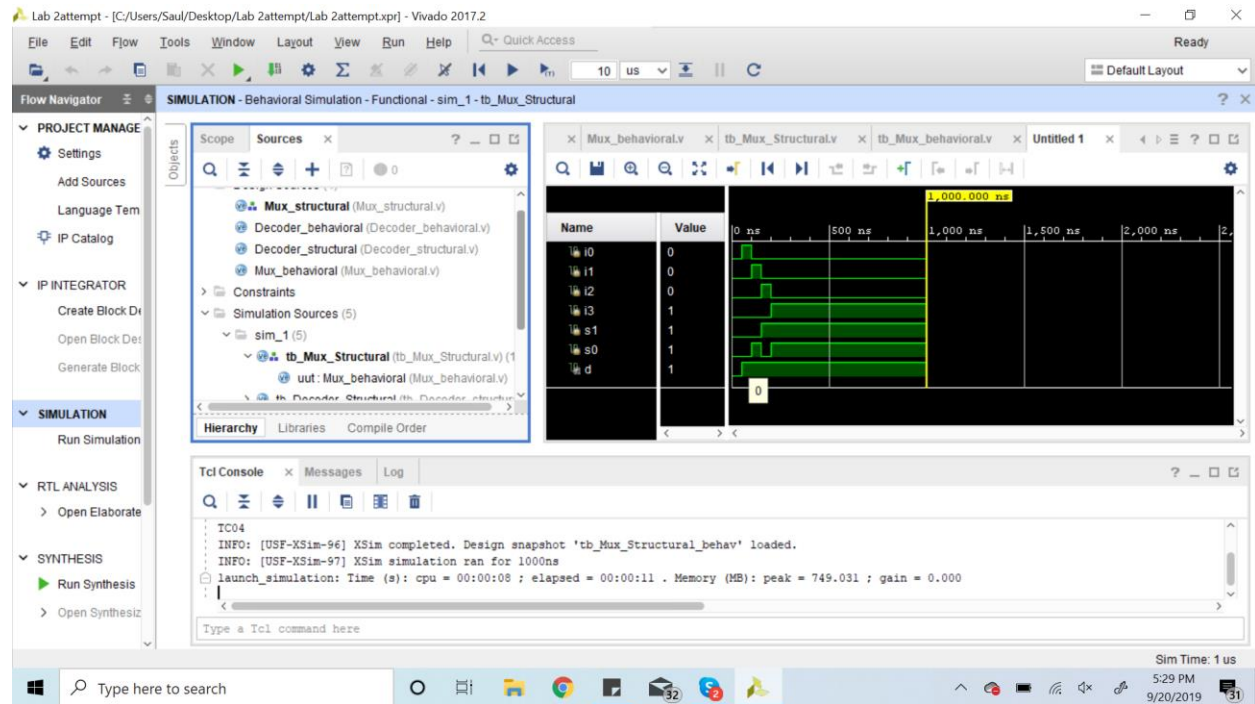

## Design Source: Mux Behavioral

```

`timescale 1ns / 1ps

```

```

module Mux_behavioral(

```

```

    input i0,

```

```

    input i1,

```

```

    input i2,

```

```

    input i3,

```

```

    input s1,

```

```

    input s0,

```

```

    output reg d

```

```

);
always @(i0,i1,i2,i3,s1,s0)
begin

d = 1'b0;

case ({i0,i1,i2,i3,s1,s0})
    6'b100000 : d = 1'b1;
    6'b010001 : d = 1'b1;
    6'b001010 : d = 1'b1;
    6'b000111 : d = 1'b1;

    default : begin
        d = 1'b0;
    end
endcase
end
endmodule

```

### **Testbench: tb\_Mux\_behavioral**

```
`timescale 1ns / 1ps
```

```
module tb_Mux_behavioral;
```

```
    reg i0;
```

```
    reg i1;
```

```
    reg i2;
```

```
    reg i3;
```

```
    reg s1;
```



```
reg s0;
```

```
wire d;
```

```
Mux_behavioral uut (
```

```
.i0(i0),
```

```
.i1(i1),
```

```
.i2(i2),
```

```
.i3(i3),
```

```
.s1(s1),
```

```
.s0(s0),
```

```
.d(d)
```

```
);
```

```
initial begin
```

```
    i0 = 0;
```

```
    i1 = 0;
```

```
    i2 = 0;
```

```
    i3 = 0;
```

```
    s1 = 0;
```

```
    s0 = 0;
```

```
    #50;
```

```
/*
```

```
    i0 = 0;
```

```
    i1 = 0;
```

```
    i2 = 0;
```

```
i3 = 0;

s1 = 0;

s0 = 0;

$display ("TC01");

if (d != 1'b0 ) $display ("Result is wrong");

#50;
```

```
i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

s1 = 0;

s0 = 1;

$display ("TC02");

if (d != 1'b0 ) $display ("Result is wrong");

#50;
```

```
i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

s1 = 1;

s0 = 0;

$display ("TC03");

if (d != 1'b0 ) $display ("Result is wrong");

#50;
```

```
i0 = 0;
```

```

i1 = 0;

i2 = 0;

i3 = 0;

s1 = 1;

s0 = 1;

$display ("TC04");

if (d != 1'b0 ) $display ("Result is wrong");

#50;

*/

i0 = 1;

i1 = 0;

i2 = 0;

i3 = 0;

s1 = 0;

s0 = 0;

$display ("TC01");

if (d != 1'b1 ) $display ("Result is wrong");

#50;


i0 = 0;

i1 = 1;

i2 = 0;

i3 = 0;

s1 = 0;

s0 = 1;

$display ("TC02");

if (d != 1'b1 ) $display ("Result is wrong");

#50;

```

```
i0 = 0;
i1 = 0;
i2 = 1;
i3 = 0;
s1 = 1;
s0 = 0;
$display ("TC03");
if (d != 1'b1 ) $display ("Result is wrong");
#50;
```

```
i0 = 0;
i1 = 0;
i2 = 0;
i3 = 1;
s1 = 1;
s0 = 1;
$display ("TC04");
if (d != 1'b1 ) $display ("Result is wrong");
```

```
end
```

```
endmodule
```

Lab 2attempt - [C:/Users/Saul/Desktop/Lab 2attempt/Lab 2attempt.xpr] - Vivado 2017.2

File Edit Flow Tools Window Layout View Run Help Quick Access Ready

Flow Navigator SIMULATION - Behavioral Simulation - Functional - sim\_1 - tb\_mux\_behavioral

PROJECT MANAGER

- Settings
- Add Sources
- Language Tem
- IP Catalog
- IP INTEGRATOR
  - Create Block D
  - Open Block Des
  - Generate Block
- SIMULATION**
  - Run Simulation
- RTL ANALYSIS
  - Open Elaborate
- SYNTHESIS
  - Run Synthesis
  - Open Synthesiz

Scope Sources x ? - □ □

Design Sources (4)

- Mux\_behavioral (Mux\_behavioral.v)
- Decoder\_behavioral (Decoder\_behavioral.v)
- Decoder\_structural (Decoder\_structural.v)
- Mux\_structural (Mux\_structural.v)

Constraints

Simulation Sources (5)

- sim\_1 (5)
  - tb\_mux\_behavioral (tb\_mux\_behavioral.v) (1)
  - tb\_decoder\_structural (tb\_decoder\_structural.v)

Hierarchy Libraries Compile Order

tb\_mux\_behavioral.v x tb\_mux\_structural.v x tb\_mux\_behavioral.v x Untitled 2 x

Name Value

i0	0
i1	0
i2	0
i3	1
s1	1
s0	1
d	1

0 ns 500 ns 1,000 ns 1,500 ns 2,000 ns 2,500 ns

1,000.000 ns


Tcl Console x Messages Log ? - □ □

INFO: [USF-XSim-96] XSim completed. Design snapshot 'tb\_mux\_behavioral\_behav' loaded.  
INFO: [USF-XSim-97] XSim simulation ran for 1000ns  
launch\_simulation: Time (s): cpu = 00:00:04 ; elapsed = 00:00:06 . Memory (MB): peak = 749.031 ; gain = 0.000

Type a Tcl command here

Sim Time: 1 us  
6:09 PM  
9/20/2019

## Part 2

 

Truth Table

$s_1$	$s_0$	$d$
0	0	$i_0$
0	1	$i_1$
1	0	$i_2$
1	1	$i_3$

Algebraic Expression

$$d = \bar{s}_1 \bar{s}_0 i_0 + \bar{s}_1 s_0 i_1 + s_1 \bar{s}_0 i_2 + s_1 s_0 i_3$$

Circuit

